



EEE240

Fundamentals of Digital Logic Design

Chapter no. 4

Dr. Ghufraan Shafiq


Assistant Professor

Department of Electrical Engineering

COMSATS University Islamabad

Review

- What is the utility of k Maps?
- For a 6 variable k Map, how many square boxes will be required?
- What is the rule for two adjacent squares in k-maps?
- What is the rule for combining the squares? i.e. rule for size of any set?
- What are implicants, prime implicants and essential prime implicants? What is the rule for getting the minimized expression?
- How do we get the expression for a complement of a function from the k-map?
- What is the advantage of considering don't care condition?

 

Outline


- Introduction to combinational logic
- Combinational circuits
- Analysis procedure
- Design procedure
- Binary adder-subtractor
- Decimal adder
- Binary multiplier
- Magnitude comparator
- Decoders
- Encoders
- Multiplexers



Must Read

Chapter No. 4: Combinational Logic

4/10/2026

 


Introduction

- Logic circuits
 - Combinational
 - Only logic gates
 - Output depends only on present combination of inputs
 - Can be specified logically by a set of Boolean functions
 - Sequential
 - Logic gates with storage elements
 - Outputs are function of inputs and state of the storage elements

Combinational Circuits

 - Output is function of input only
i.e. no feedback




When **input** changes, **output** may change (after a delay)

Combinational Circuits


- Analysis

 - Given a circuit, find out its *function*
- Function may be expressed as:
 - Boolean function
 - Truth table




- Design

 - Given a desired function, determine its *circuit*
- Function may be expressed as:
 - Boolean function
 - Truth table




Analysis Procedure

- Boolean Expression Approach

 

Analysis Procedure


- Truth Table Approach

 

A	B	C	F ₁	F ₂
0	0	0	0	0

Analysis Procedure


- Truth Table Approach

 

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0

Analysis Procedure


- Truth Table Approach

 

A	B	C	F ₁	F ₂
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0

Analysis Procedure


- Truth Table Approach

 

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1

Analysis Procedure


- Truth Table Approach

 

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0

Analysis Procedure


- Truth Table Approach

 

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1

Analysis Procedure


- Truth Table Approach

 

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1

Analysis Procedure

- Truth Table Approach

 

A	B	C	F_1	F_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

	B			
	0	1	0	1
A	1	0	1	0
	C			

	B			
	0	0	1	0
A	0	1	1	1
	C			

$$F_1 = AB'C' + A'BC' + A'B'C + ABC$$


$$F_2 = AB + AC + BC$$

Design Procedure

- Given a problem statement:
 - Determine the number of *inputs* and *outputs*
 - Derive the truth table
 - Simplify the Boolean expression for each output
 - Produce the required circuit

 Example:


Design a circuit to convert a “BCD” code to “Excess 3” code




Design Procedure

- BCD-to-Excess 3 Converter


<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

 


$$w = A + BC + BD$$

 

$$x = B'C + B'D + BC'D'$$

 

$$y = C'D' + CD$$

 


$$z = D'$$

Design Procedure

- BCD-to-Excess 3 Converter

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	x	x	x	x
1	0	1	1	x	x	x	x
1	1	0	0	x	x	x	x
1	1	0	1	x	x	x	x
1	1	1	0	x	x	x	x
1	1	1	1	x	x	x	x

 

$$w = A + B(C+D)$$




$$y = (C+D)' + CD$$

$$x = B'(C+D) + B(C+D)'$$

$$z = D'$$

Seven-Segment Decoder

<i>w x y z</i>	<i>a b c d e f g</i>
0 0 0 0	1 1 1 1 1 1 0
0 0 0 1	0 1 1 0 0 0 0
0 0 1 0	1 1 0 1 1 0 1
0 0 1 1	1 1 1 1 0 0 1
0 1 0 0	0 1 1 0 0 1 1
0 1 0 1	1 0 1 1 0 1 1
0 1 1 0	1 0 1 1 1 1 1
0 1 1 1	1 1 1 0 0 0 0
1 0 0 0	1 1 1 1 1 1 1
1 0 0 1	1 1 1 1 0 1 1
1 0 1 0	x x x x x x x
1 0 1 1	x x x x x x x
1 1 0 0	x x x x x x x
1 1 0 1	x x x x x x x
1 1 1 0	x x x x x x x
1 1 1 1	x x x x x x x

   

$$a = w + y + xz + x'z'$$

$$b = \dots$$


$$c = \dots$$

$$d = \dots$$




Binary Adder

 - Half Adder
 - Adds 1-bit plus 1-bit
 - Produces Sum and Carry




$$\begin{array}{r} x \\ + y \\ \hline C \quad S \end{array}$$

x y	C S
0 0	0 0
0 1	0 1
1 0	0 1
1 1	1 0

 

Binary Adder

 - Full Adder
 - Adds 1-bit plus 1-bit plus 1-bit
 - Produces Sum and Carry



x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

	y			
	0	1	0	1
x	1	0	1	0
	z			

$$S = xy'z' + x'yz' + x'y'z + xyz = x \oplus y \oplus z$$

	y			
	0	0	1	0
x	0	1	1	1
	z			

$$C = xy + xz + yz$$

$$\begin{array}{r}
 x \\
 + y \\
 + z \\
 \hline
 C \quad S
 \end{array}$$

Binary Adder

- Full Adder

$$S = xy'z' + x'yz' + x'y'z + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

